

American International University- Bangladesh
Faculty of Engineering
Computer Aided Design and Drafting Lab
Midterm assignment (Summer 2020-2021)

Marks:30

Submission due date: 01/07/2021

Instructions:

1. Draw the electrical circuits in Auto-Cad maintaining all the text visible in the circuit diagram.
2. Create PDF of Auto-Cad files and submit the PDF files NOT screenshot or Auto-Cad file.
3. Mention your group number and group members ID using text option of Auto-Cad.
4. Only one group member will submit the assignment file to me through email (email subject CAD [Section] Assignment) , but all the group members should contribute while drawing.





